



COLLÈGE  
DE FRANCE  
—1530—



Chaire de Physique Mésoscopique  
Michel Devoret  
Année 2011, 10 mai - 21 juin

## **AMPLIFICATION ET RETROACTION QUANTIQUES**

### ***QUANTUM AMPLIFICATION AND FEEDBACK***

Seconde Leçon / *Second Lecture*

Transparents des leçons disponibles à <http://www.physinfo.fr/lectures.html>

11-II-1

### **PROGRAM OF THIS YEAR'S LECTURES**

Lecture I: Introduction to quantum-limited amplification and feedback

Lecture II: How do we model open, out-of-equilibrium, non-linear quantum systems?

Lecture III: Is it possible to optimize the parametric amplifier characteristics while maintaining its noise at the quantum limit?

Lecture IV: What are the minimal requirements for an active circuit to be fully directional and noiseless?

Lecture V: Can continuous quantum measurements be viewed as a form of Brownian motion?

Lecture VI: How can we maintain a dynamic quantum state alive?

Please note that there will be no lecture on May 24

11-II-2

## CALENDAR OF SEMINARS

**May 10: Fabien Portier, SPEC-CEA Saclay**  
The Bright Side of Coulomb Blockade

**May 17, 2011: Jan van Ruitenbeek (Leiden University, The Netherlands)**  
Quantum Transport in Single-molecule Systems

**May 31, 2011: Irfan Siddiqi (UC Berkeley, USA)**  
Quantum Jumps of a Superconducting Artificial Atom

**June 7, 2011: David DiVicenzo (IQI Aachen, Germany)**  
Quantum Error Correction and the Future of Solid State Qubits

**June 14, 2011: Andrew Cleland (UC Santa Barbara, USA)**  
Images of Quantum Light

**June 21, 2011: Benjamin Huard (LPA - ENS Paris)**  
Building a Quantum Limited Amplifier from Josephson Junctions and Resonators

**June 21, 2011 (3pm): Andrew Cleland (UC Santa Barbara, USA)**  
How to Be in Two Places at the Same Time ?

11-II-3

## LECTURE II : MODELLING OPEN, OUT-OF-EQUILIBRIUM, NON-LINEAR QUANTUM CIRCUITS


### OUTLINE

1. Modes of isolated, linear quantum circuits, non-linear processes
2. Open, out-of-equilibrium, linear systems: input-output theory
3. Characterizing non-linear elements, participation ratio

11-II-4


## CLOSED, NON-DISSIPATIVE LINEAR CIRCUITS

Example:

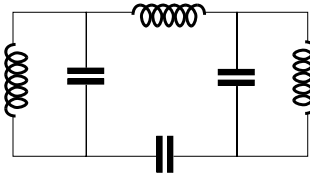

- just inductances and capacitances
- no sources and no resistances
- undamped normal modes
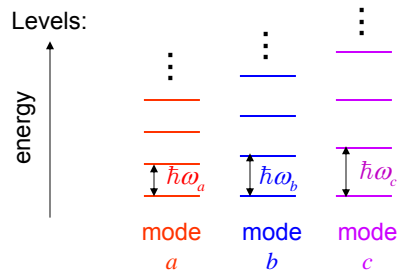
# of modes = # independent pairs of capacitances and inductances



Hamiltonian:

$$H = \hbar\omega_a a^\dagger a + \hbar\omega_b b^\dagger b + \hbar\omega_c c^\dagger c$$


$$= \sum_{m=a,b,c} \hbar\omega_m a_m^\dagger a_m$$

$m$  : normal mode index

$a_m$  : normal mode amplitude

11-II-5

## LUMPED ELEMENTS MICROWAVE CIRCUITS

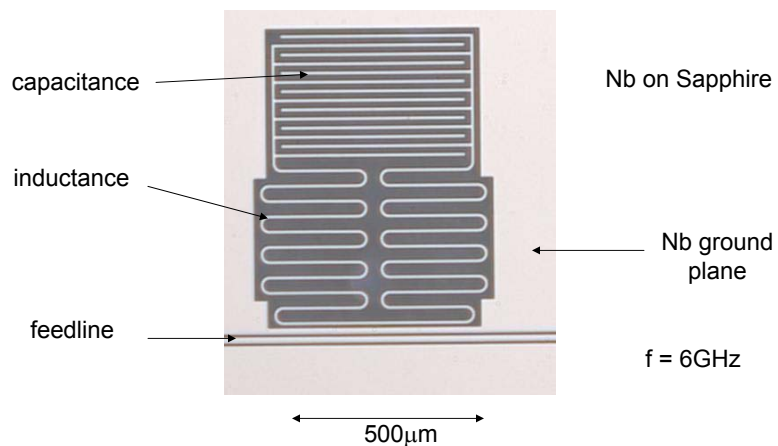


11-II-6

## HAMILTONIAN FROM CHARGES AND FLUXES

Use loop variables:

$$\Phi_i^{loop} = \int_{-\infty}^t V_i^{ind} dt_1$$
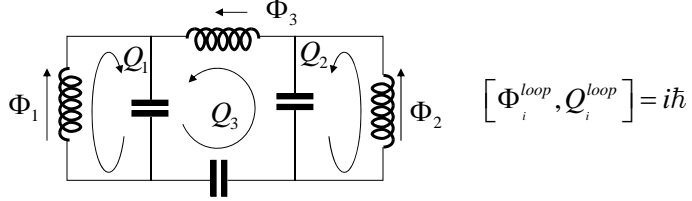
$$Q_i^{loop} = \int_{-\infty}^t I_i^{cap} dt_1$$



Hamiltonian: 
$$H = \frac{\Phi_1^2}{2L_1} + \frac{\Phi_2^2}{2L_2} + \frac{\Phi_3^2}{2L_3} + \frac{(Q_1 + Q_3)^2}{2C_1} + \frac{(Q_2 - Q_3)^2}{2C_2} + \frac{Q_3^2}{2C_3}$$


Inverse-Capacitance matrix: 
$$C_{ij}^{-1} = \frac{\partial^2 H}{\partial Q_i \partial Q_j} \quad \dot{\Phi}_i = V_i = \sum_j C_{ij}^{-1} Q_j$$

Inverse-Inductance matrix: 
$$\mathcal{L}_{ij}^{-1} = \frac{\partial^2 H}{\partial \Phi_i \partial \Phi_j} \quad \dot{Q}_i = I_i = -\sum_j \mathcal{L}_{ij}^{-1} \Phi_j$$

11-II-7

## COMMUTATION RELATION OF FLUXES AND CHARGES

E.M. Lagrangian:

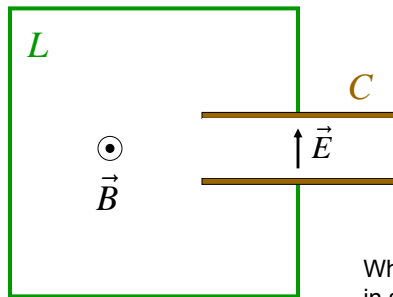

$$\iiint_{vol} \frac{dv}{2} (\epsilon_0 E^2 - \mu_0^{-1} B^2)$$

$$= \iiint_{vol} \frac{dv}{2} \left( \epsilon_0 \left( \frac{\partial \vec{A}}{\partial t} \right)^2 - \mu_0^{-1} (\vec{\nabla} \times \vec{A})^2 \right)$$

vector potential  
= field amplitude

When magnetic and electric fields do not coexist in space (lumped elements), hamiltonian of corresponding mode is given by:

$$H = \frac{Q_{cap}^2}{2C} + \frac{\Phi_{ind}^2}{2L}$$

11-II-8

## CURRENTS AND VOLTAGES OF NORMAL MODES

Equation of motions in matrix form:

$$V = \dot{\Phi} = \mathcal{C}^{-1}Q$$

$$I = \dot{Q} = -\mathcal{L}^{-1}\Phi$$

positive symmetric

Matrix of eigenfrequencies

$$\Omega = \left( \mathcal{L}^{-1/2} \mathcal{C}^{-1} \mathcal{L}^{-1/2} \right)^{1/2}$$

$$\Omega = O \begin{pmatrix} \omega_a & 0 & 0 \\ 0 & \omega_b & 0 \\ 0 & 0 & \omega_c \end{pmatrix} O^{-1}$$

orthogonal

Impedance matrix

$$Z = \mathcal{L}^{+1/4} \mathcal{C}^{-1/2} \mathcal{L}^{+1/4}$$

$$Z = O^{-1} \begin{pmatrix} Z_a & 0 & 0 \\ 0 & Z_b & 0 \\ 0 & 0 & Z_c \end{pmatrix} O$$

$$\Phi = O \sqrt{\frac{\hbar Z}{2}} (a + a^\dagger)$$

$$Q = O \sqrt{\frac{\hbar}{2Z}} \begin{pmatrix} a - a^\dagger \\ i \end{pmatrix}$$

column vectors

1 photon  
@ f=10GHz  
Z=100Ω





$\delta V \sim 1\mu\text{V}$   
 $\delta I \sim 10\text{nA}$

11-II-9
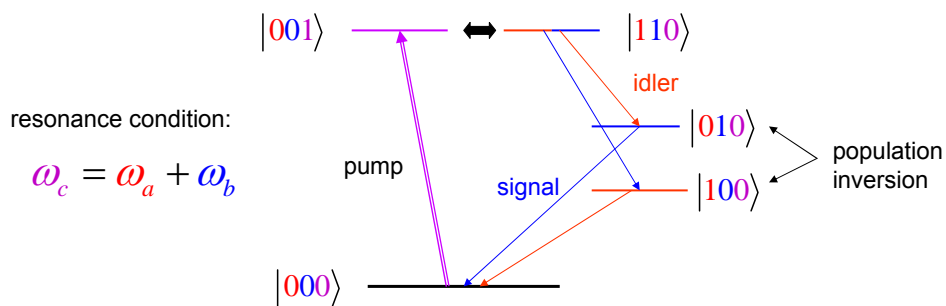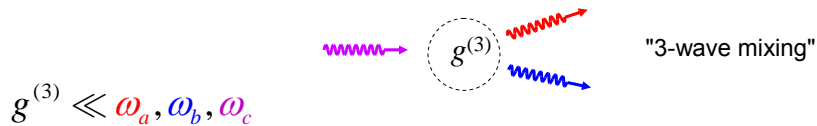
## AMPLIFICATION EXPLOITS COMBINATION OF ANHARMONICITY, DRIVE AND DAMPING

$$H = \hbar\omega_a a^\dagger a + \hbar\omega_b b^\dagger b + \hbar\omega_c c^\dagger c + [\hbar g^{(3)} a^\dagger b^\dagger c + \text{h.c.}]$$



11-II-10

UNDERSTANDING OF AMPLICATION INVOLVES  
JOINT TREATMENT OF:

1. STEADY-STATE OUT-OF-EQUILIBRIUM
2. NON-LINEAR PROCESSES


11-II-11

**OUTLINE**


1. Modes of isolated, linear quantum circuits, non-linear processes
2. Open, out-of-equilibrium, linear systems: input-output theory
3. Characterizing non-linear elements, participation ratio

11-II-4
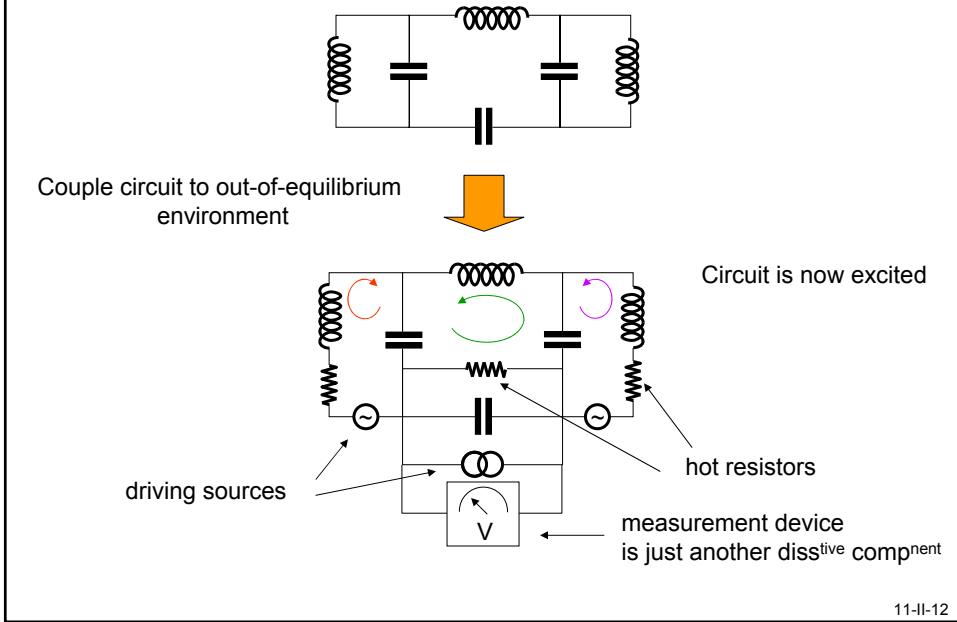
## OPEN, DRIVEN, DISSIPATIVE LINEAR CIRCUITS




## OPEN, DISSIPATIVE LINEAR CIRCUITS

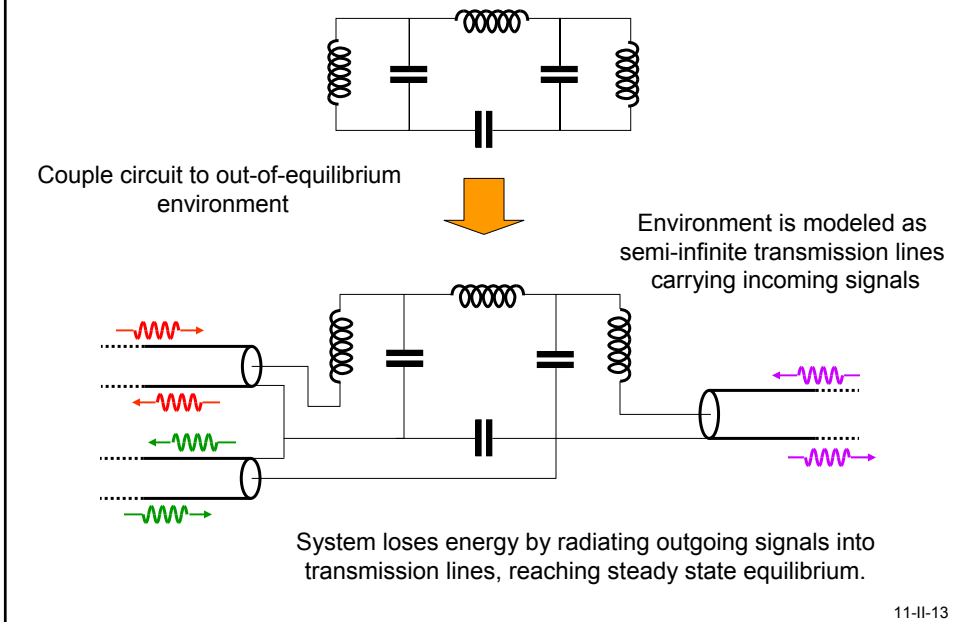
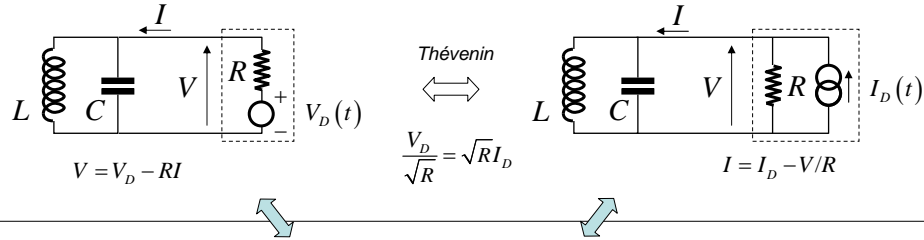
## CORRESPONDANCE BETWEEN DRIVE AND INPUT FIELDS, DISSIPATION AND LINE IMPEDANCE

Dissipative drive being equivalent to semi-infinite transmission line with incoming signals, system dynamics is described by relation between input and output fields




$$A^{in}(t) = \frac{V}{2\sqrt{R}} + \frac{\sqrt{R}I}{2}$$

$$= \frac{V_D}{2\sqrt{R}} = \frac{\sqrt{R}I_D}{2}$$

$$A^{out}(t) = \frac{V}{2\sqrt{R}} - \frac{\sqrt{R}I}{2}$$

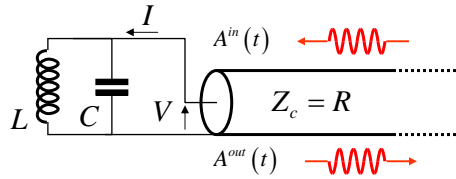
$$= \frac{V}{\sqrt{R}} - A^{in}(t) = A^{in}(t) - \sqrt{R}I$$



Information carried by outgoing signal corresponds to that acquired by a volt- or an ammeter

11-II-14
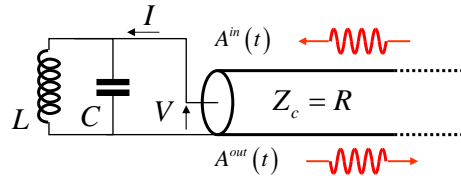
## PRINCIPLE OF INPUT-OUTPUT CALCULATIONS



Hamiltonian of circuit  $\rightarrow$  functional relation between I and V:  $f\{I(t), V(t)\} = 0$

Here, for the LC circuit, we obtain:  $\frac{d}{dt}I(t) = \left(C \frac{d^2}{dt^2} + \frac{1}{L}\right)V(t)$

In this relation, we now operate the substitution:

$$V = \sqrt{R}[A^{in} + A^{out}]$$

$$I = \frac{1}{\sqrt{R}}[A^{in} - A^{out}]$$

Expressing the outgoing field in terms of the incoming fields, we obtain the input-output relations.

For our example:  $C\ddot{A}^{out} + \frac{1}{R}\dot{A}^{out} + \frac{1}{L}A^{out} = -C\ddot{A}^{in} + \frac{1}{R}\dot{A}^{in} - \frac{1}{L}A^{in}$

11-II-15



## FOURIER TRANSFORMS OF FIELDS


Starting from time-domain expression  $C\ddot{A}^{out} + \frac{1}{R}\dot{A}^{out} + \frac{1}{L}A^{out} = -C\ddot{A}^{in} + \frac{1}{R}\dot{A}^{in} - \frac{1}{L}A^{in}$

and introducing Fourier transforms  $A^{in/out}[\omega] = \frac{1}{\sqrt{2\pi}} \int_{-\infty}^{+\infty} e^{i\omega t} A^{in/out}(t) dt$

We obtain:  $A^{iout}[\omega] = \left( \frac{-y(\omega)+1}{y(\omega)+1} \right) A^{in}[\omega]$        $y(\omega) = R \left( iC\omega + \frac{1}{iL\omega} \right) = i \frac{\omega^2 - \omega_0^2}{\gamma\omega}$


↑ unity modulus      ↑ reduced admittance (purely imaginary)      ↑ resonance frequency  
↑ damping rate

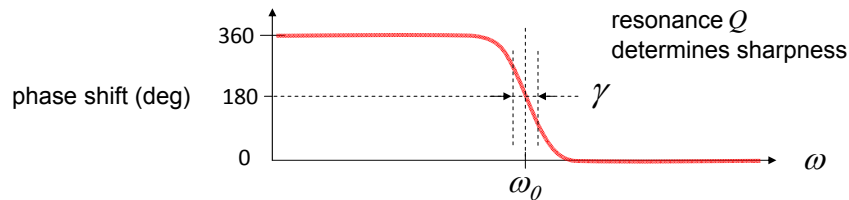When resonance quality factor  $Q = \frac{\omega_0}{\gamma} \gg 1$     RWA  $y(\omega) = i \frac{\omega - \omega_0}{\gamma/2}$



11-II-15
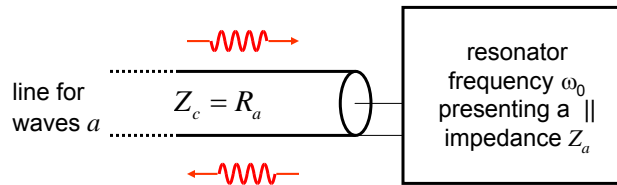
## PHYSICAL MEANING OF DAMPING RATE IN INPUT-OUTPUT PICTURE




Propagating photons @ frequency  $\omega_0$  enter the resonator and reside a time  $\gamma^{-1}$  as standing waves before being re-radiated back.

$$\gamma = \frac{R_a}{Z_a} \omega_0 = R_a Y_a \omega_0$$

↑ environment      ↑ resonator

11-II-16

## SCATTERING MATRIX FOR A LINEAR SYSTEM

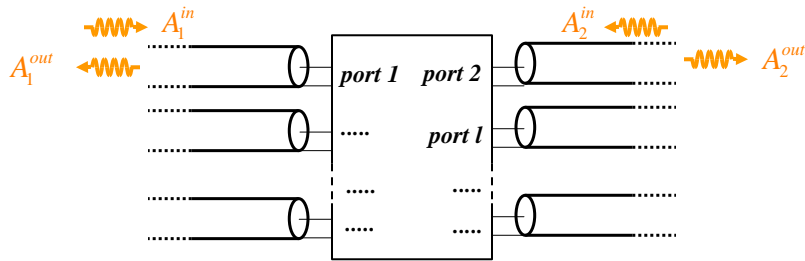

$$\begin{bmatrix} A_1^{out}[\omega] \\ A_2^{out}[\omega] \\ \dots \\ A_l^{out}[\omega] \\ \dots \end{bmatrix} = \begin{bmatrix} s_{11}[\omega] & s_{12}[\omega] & \dots & s_{1l}[\omega] & \dots \\ s_{21}[\omega] & s_{22}[\omega] & \dots & s_{2l}[\omega] & \dots \\ \dots & \dots & \dots & \dots & \dots \\ s_{l1}[\omega] & s_{l2}[\omega] & \dots & s_{ll}[\omega] & \dots \\ \dots & \dots & \dots & \dots & \dots \end{bmatrix} \begin{bmatrix} A_1^{in}[\omega] \\ A_2^{in}[\omega] \\ \dots \\ A_l^{in}[\omega] \\ \dots \end{bmatrix}$$

↑ OUTGOING AMPLITUDES      "S" PARAMETERS, SCATTERING MATRIX      ↑ INCOMING AMPLITUDES

all components are at same frequency!  
will change for amplifier

11-II-17

## WAVE AMPLITUDE vs PHOTON OPERATORS

operator of wave amplitude in Fourier domain

propagation direction

$$A^{in,out}[\omega] = \sqrt{\frac{\hbar|\omega|}{2}} a^{in,out}[\omega]$$

angular frequency (positive or negative)

$$\begin{cases} [A[\omega]] = [\text{power}^{1/2} \times \text{time}] = [\text{action}]^{1/2} \\ [a[\omega]] = [\text{time}]^{1/2} \end{cases}$$

field ladder operator

$$a[-\omega] = a[\omega]^\dagger$$

Ladder operators have commutation relations:

$$[a^{in,out}[\omega_1], a^{in,out}[\omega_2]] = \text{sgn}(\omega_1 - \omega_2) \delta(\omega_1 + \omega_2)$$

Scattering always preserves commutation relations

11-II-18

## NUMBER OF PHOTONS IN INPUT SIGNAL

Wave amplitude spectral density:

$$\langle A[\omega_1]A[\omega_2] \rangle = S_{AA}[\omega_1]\delta(\omega_1 + \omega_2) \quad \text{In } T \text{ equilibrium: } S_{A^in A^in}[\omega] = \frac{\hbar\omega}{4} \left[ \coth\left(\frac{\hbar\omega}{2k_B T}\right) + 1 \right]$$

$$[S_{AA}[\omega]] = [\text{energy}]$$

$$S_{A^in A^in}[\omega] \xrightarrow{T \rightarrow \infty} \frac{k_B T}{2}$$

Photon amplitude spectral density:


$$\langle a[\omega_1]a[\omega_2] \rangle = S_{aa}[\omega_1]\delta(\omega_1 + \omega_2)$$

Number of photons per unit time per unit bandwidth crossing a section of line:

$$N_a(|\omega|) = S_{aa}[+|\omega|] + S_{aa}[-|\omega|]$$

In thermal equilibrium:

$$\begin{cases} N_{a^in}^T(|\omega|) = \frac{1}{2} \coth\left(\frac{\hbar|\omega|}{2k_B T}\right) \\ N_{a^in}^T(|\omega|) \xrightarrow{T \rightarrow \infty} \frac{k_B T}{\hbar|\omega|} \\ N_{a^in}^T(|\omega|) \xrightarrow{T \rightarrow 0} \frac{1}{2} \end{cases}$$

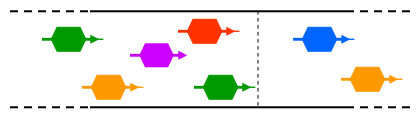

N.B.: Link between "engineer" and "physicist" spectral densities

$$\mathcal{S}_{XX}[\nu] = S_{XX}[\omega = 2\pi\nu] + S_{XX}[\omega = -2\pi\nu]$$

standard frequency in Hz

11-II-19

## SCATTERING MATRIX FOR PASSIVE LINEAR CIRCUIT

When circuit contains only linear capacitances and inductances:

$$S[\omega] = \left( Z_c^{1/2} Y[\omega] Z_c^{1/2} + 1 \right)^{-1} \left( -Z_c^{1/2} Y[\omega] Z_c^{1/2} + 1 \right)$$

Admittance matrix of circuit  
Gives current in port k as function of voltages in port l. Can be computed directly from hamiltonian.

Diagonal matrix of line impedances

This expression is a generalization of the formula for reflection on a load:

$$r = \frac{Z_L - Z_c}{Z_L + Z_c}$$

Y matrix is i times a positive hermitian matrix



unitarity of S matrix

$$S^\dagger S = 1$$

information conservation  
energy conservation

Another property, fully general:

causality



POLES OF S MATRIX IN LOWER-HALF PLANE

11-II-20

## EXAMPLE: INPUT-OUTPUT TREATMENT OF DISPERSIVE REFLECTION ATTENUATOR

$C_{a,b} \ll C$

$s_{aa}(\omega)$  — attenuation of reflected signal

$$S = \begin{bmatrix} \frac{\Gamma_a - \Gamma_b - i\Delta\omega}{\Gamma_a + \Gamma_b + i\Delta\omega} & -\frac{2\Gamma_a^{1/2}\Gamma_b^{1/2}}{\Gamma_a + \Gamma_b + i\Delta\omega} \\ -\frac{2\Gamma_a^{1/2}\Gamma_b^{1/2}}{\Gamma_a + \Gamma_b + i\Delta\omega} & \frac{\Gamma_b - \Gamma_a - i\Delta\omega}{\Gamma_a + \Gamma_b + i\Delta\omega} \end{bmatrix}$$

$$\Gamma_{a,b} = \frac{\gamma_{a,b}}{2} \cong \frac{R_{a,b}C_{a,b}^2}{4LC^2}$$

$$\Delta\omega = \omega - \omega_0$$

Interference: when  $\Delta\omega = 0$  &  $\gamma_a = \gamma_b$ , reflection vanishes!

Added noise by attenuator in reflection of  $a$ : (referred to input)  $\mathcal{A} = N_b \frac{|s_{ab}|^2}{|s_{aa}|^2} = N_b (|s_{aa}|^{-2} - 1)$


11-II-21

### OUTLINE

1. Modes of isolated, linear quantum circuits, non-linear processes
2. Open, out-of-equilibrium, linear systems: input-output theory
3. Characterizing non-linear elements, participation ratio

11-II-4
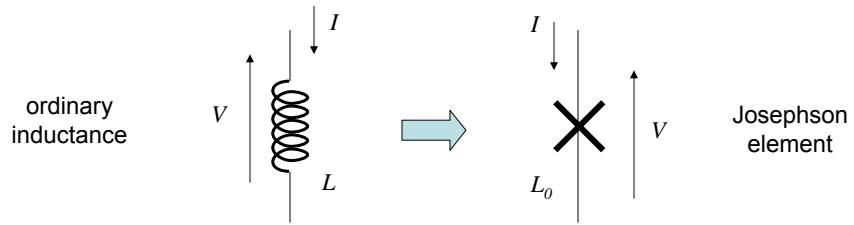
## JE = NON-DISSIPATIVE, NON-LINEAR INDUCTANCE



$$V(t) = L \frac{dI(t)}{dt}$$

$$V(t) = \phi_0 \frac{d}{dt} \sin^{-1} \frac{I(t)}{I_0} \quad \phi_0 = \frac{\hbar}{2e}$$

current-dependence of inductance  $\longrightarrow$


$$= \frac{\phi_0}{I_0} \frac{1}{\sqrt{1 - \frac{I(t)^2}{I_0^2}}} \frac{dI(t)}{dt}$$

Energy stored in Josephson element:  $E(t) = \int_0^{I(t)} V(t) dI = E_J \left( 1 - \cos \left[ \sin^{-1} \frac{I(t)}{I_0} \right] \right)$

$E_J = \phi_0 I_0$

11-II-22

## CHARACTERIZING NON-LINEARITY

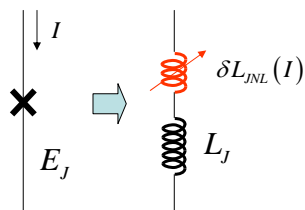

$$L_J = \frac{\hbar^2}{(2e)^2 E_J}$$


$$\delta L_{JNL} = L_J \left[ \left( 1 - \frac{I^2}{I_0^2} \right)^{-1/2} - 1 \right]$$

$$= \frac{1}{2} L_J \frac{I^2}{I_0^2} + O\left(\frac{I^4}{I_0^4}\right)$$

$$\boxed{\times} \quad E = \omega(E) = \sqrt{\frac{1}{L(E)C}}$$


Anharmonicity
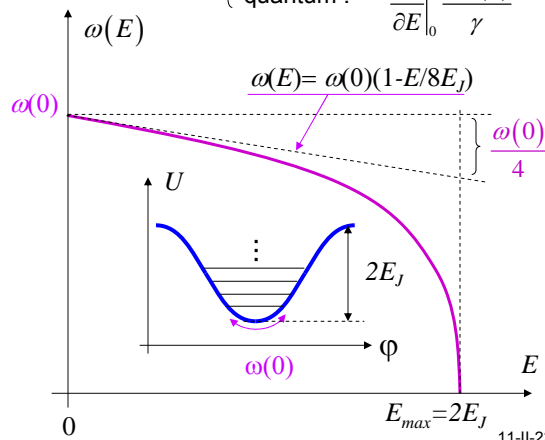
$$\begin{cases} \text{classical : } \frac{\partial \omega}{\partial E_0} \frac{E_{\max}}{\omega(0)} = \frac{1}{4} \\ \text{quantum : } \frac{\partial \omega}{\partial E_0} \frac{\hbar \omega(0)}{\gamma} \end{cases}$$



11-II-23


## SQUID's: MODULATION OF NON-LINEARITY

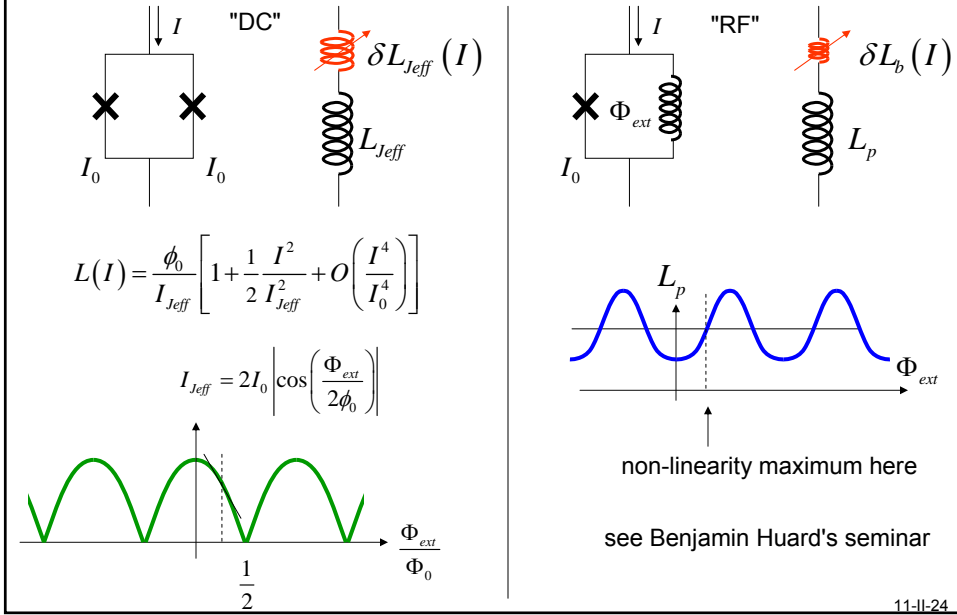

## EVALUATION OF $g^{(3)}$

$I_0 \sim 10\mu\text{A} \Rightarrow L_J \sim 30\text{pH}$   
 $\Rightarrow E_J/h \sim 5\text{THz}$

$f \sim 5\text{GHz}, Z \sim 1\Omega$

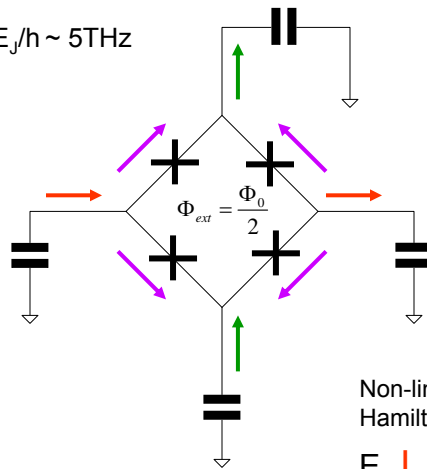


$1 \text{ photon} \sim 100\text{nA}$   
 $\sim I_0/100$

Non-linear term in Hamiltonian is of order:

$$\frac{E_J I_x I_y I_z}{(I_0)^3} \Rightarrow g^{(3)} \sim \text{MHz}$$


11-II-25

## DILUTION OF NON-LINEARITY

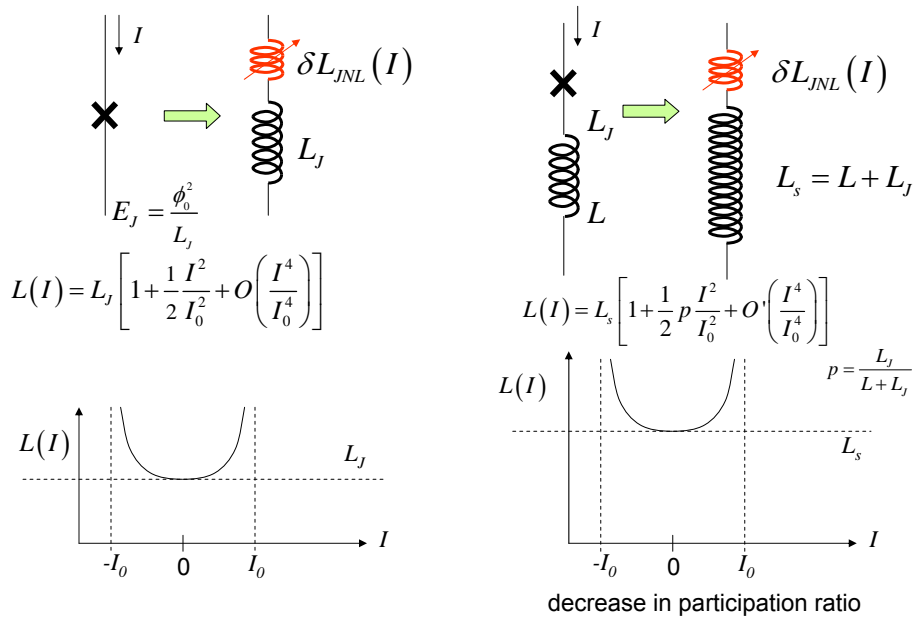

11-II-26


## BANDWIDTH OF NON-LINEARITY

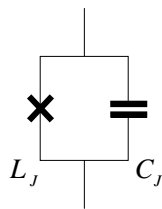

$$\omega_p = \sqrt{\frac{1}{L_J C_J}}$$

Plasma frequency is ultimate bandwidth limitation (20-30GHz)

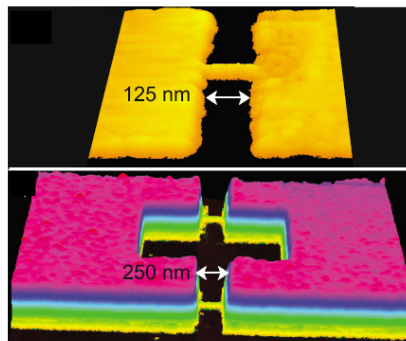Nanobridges have a higher plasma frequency than tunnel junctions and are promising non-linear elements for superconducting amplifiers.



Vijay et al.  
Appl Phys. Lett.  
**96**, 223112  
(2010)

11-II-29

## SELECTED BIBLIOGRAPHY

### Books and series of lectures

- Braginsky, V. B., and F. Y. Khalili, "Quantum Measurements" (Cambridge University Press, Cambridge, 1992)
- Clarke, J. and Braginsky, A. I., eds., "The SQUID Handbook" (Wiley-VCH, Weinheim, Germany, 2006)
- Esteve, D., Raimond, J.-M., and Dalibard J., "Quantum Entanglement and Information Processing" (Elsevier, Amsterdam, 2004)
- Gardiner, C.W. and Zoller, P. "Quantum Noise" (Springer, Berlin, 2004)
- Haroche, S., Lectures at College de France, 2011
- Haroche, S. and Raimond, J.-M., "Exploring the Quantum" (Oxford University Press, 2006)
- Nielsen, M. and Chuang, I., "Quantum Information and Quantum Computation" (Cambridge, 2001)
- Walls, D.F., and Milburn, G.J. "Quantum Optics" (Springer, Berlin, 2008)
- Wiseman, H.M. and Milburn, G.J., "Quantum Measurement and Control" (Cambridge, 2011)

### Articles

- Blais A., Gambetta J., Wallraff A., Schuster D. I., Girvin S., Devoret M.H., Schoelkopf R.J., Phys. Rev. (2007) A **75**, 032329
- Clarke, J. and Wilhelm, F. K., "Superconducting quantum bits". Nature **453**, 1031–1042 (2008).
- Clerk A. A., Devoret M. H., Girvin S. M., Marquardt F., and Schoelkopf R. J., "Introduction to Quantum Noise, Measurement and Amplification", Rev. Mod. Phys. **82**, 1155 (2010).
- Devoret, M. H., Wallraff A., and Martinis J. M., e-print cond-mat/0411174
- Schoelkopf, R.J., and Girvin, S.M., "Wiring up quantum systems," Nature **451**, 664 (2008).
- R. Vijay, M. H. Devoret, and I. Siddiqi, "Invited Review Article: The Josephson bifurcation amplifier," Review of Scientific Instruments **80**, 111101 (2009)
- R. Vijay, D. H. Slichter, and I. Siddiqi, "Observation of Quantum Jumps in a Superconducting Artificial Atom," Phys. Rev. Lett. **106**, 110502 (2011).
- Q. Zhang, R. Ruskov, and A.N. Korotkov "Continuous quantum feedback of coherent oscillations in a solid-state qubit" Phys. Rev. **B 72**, 245322 (2005).

11-II-30

END OF LECTURE