



COLLÈGE
DE FRANCE
—1530—



Chaire de Physique Mésoscopique
Michel Devoret
Année 2008, 13 mai - 24 juin

CIRCUITS ET SIGNAUX QUANTIQUES

QUANTUM SIGNALS AND CIRCUITS

Première leçon / *First Lecture*

This College de France document is for consultation only. Reproduction rights are reserved.

08-I-1

VISIT THE WEBSITE OF THE CHAIR OF MESOSCOPIC PHYSICS

<http://www.college-de-france.fr>

and follow links to:

<http://www.physinfo.fr/lectures.html>

[PDF FILES OF ALL LECTURES WILL BE POSTED ON THIS WEBSITE](#)

Questions, comments and corrections are welcome!

08-I-2

CALENDAR OF SEMINARS

[May 13: Denis Vion, \(Quantronics group, SPEC-CEA Saclay\)](#)

Continuous dispersive quantum measurement of an electrical circuit

[May 20: Bertrand Reulet \(LPS Orsay\)](#)

Current fluctuations : beyond noise

[June 3: Gilles Montambaux \(LPS Orsay\)](#)

Quantum interferences in disordered systems

[June 10: Patrice Roche \(SPEC-CEA Saclay\)](#)

Determination of the coherence length in the Integer Quantum Hall Regime

[June 17: Olivier Buisson, \(CRTBT-Grenoble\)](#)

A quantum circuit with several energy levels

[June 24: Jérôme Lesueur \(ESPCI\)](#)

High Tc Josephson Nanojunctions: Physics and Applications

NOTE THAT THERE IS NO LECTURE AND NO SEMINAR ON MAY 27 !

08-I-3

PROGRAM OF THIS YEAR'S LECTURES

Lecture I: Introduction and overview

Lecture II: Modes of a circuit and propagation of signals

Lecture III: The "atoms" of signal

Lecture IV: Quantum fluctuations in transmission lines

Lecture V: Introduction to non-linear active circuits

Lecture VI: Amplifying quantum signals with dispersive circuits

NEXT YEAR: STRONGLY NON-LINEAR AND/OR DISSIPATIVE CIRCUITS

08-I-4

LECTURE I : INTRODUCTION AND OVERVIEW

1. Review of classical radio-frequency circuits
2. Quantum information processing
3. Quantum-mechanical LC oscillator
4. A non-dissipative, non-linear element: the Josephson junction
5. Energy levels and transitions of the Cooper Pair Box
6. Summary of questions addressed by this course

08-I-5

CLASSICAL RADIO-FREQUENCY CIRCUITS

Communications



Hergé, Moulinart

1940's : MHz



2000's : GHz

Computation




US Army Photo




Sony

08-I-6

SIMPLEST EXAMPLE :

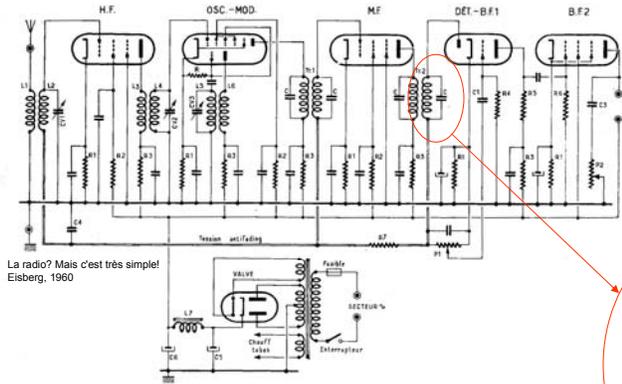

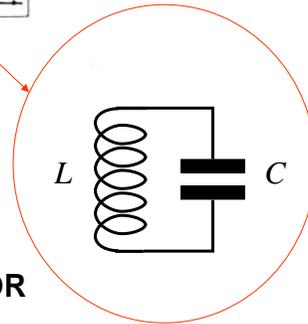La radio? Mais c'est très simple!
Eisberg, 1960




THE LC OSCILLATOR

08-1-7

WHAT IS A RADIO-FREQUENCY CIRCUIT?

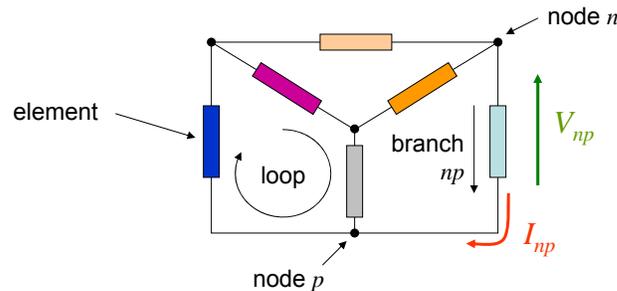A RF CIRCUIT IS A NETWORK OF ELECTRICAL ELEMENTS



TWO DYNAMICAL VARIABLES CHARACTERIZE THE STATE OF EACH DIPOLE ELEMENT AT EVERY INSTANT:


Voltage across the element: $V_{np}(t) = \int_n^p \vec{E} \cdot d\vec{\ell}$

Current through the element: $I_{np}(t) = \iint \vec{j} \cdot d\vec{\sigma}_{np}$


Signals:
any linear
combination
of these variables

08-1-8

KIRCHHOFF'S LAWS

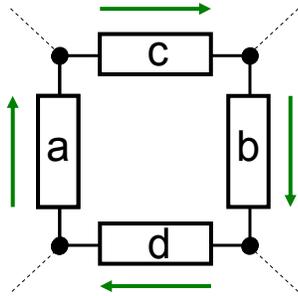
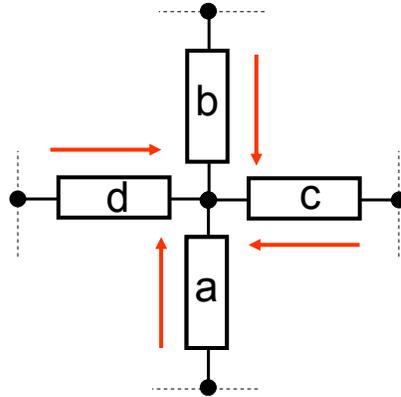
$$\sum_{\text{branches } \lambda \text{ around loop}} V_{\lambda} = 0$$



$$\sum_{\text{branches } \nu \text{ tied to node}} I_{\nu} = 0$$

08-1-9

CONSTITUTIVE RELATIONS

EACH ELEMENT IS TAKEN FROM A FINITE SET OF ELEMENT TYPES
 EACH ELEMENT TYPE IS CHARACTERIZED BY A RELATION BETWEEN
 VOLTAGE AND CURRENT

LINEAR	NON-LINEAR
inductance: $V = L \, dI/dt$	diode: $I = G(V)$
capacitance: $I = C \, dV/dt$	transistor: $I_{ds} = G(I_{gs}, V_{ds}, I_{gs}) V_{ds}$ $I_{gs} = 0$
resistance: $V = R I$	⋮ ⋮ ⋮


08-1-10

GENERALIZATIONS: MULTIPOLES, PORTS


AN ELEMENT CAN BE CONNECTED TO MORE THAN TWO NODES



dipole

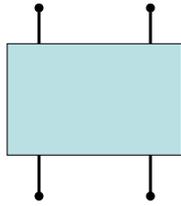

quadrupole

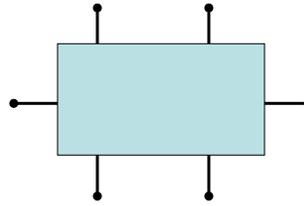

hexapole

etc....

n poles \rightarrow $\begin{cases} n-1 \text{ currents} \\ n-1 \text{ voltages} \end{cases}$

ALSO, CONSTITUTIVE RELATION OF ELEMENT NEED NOT BE LOCAL IN TIME

WILL DEAL WITH THESE HIGHER DEGREES OF COMPLEXITY LATER

08-l-11

COMPUTING THE DYNAMICAL STATE OF A CIRCUIT IN CLASSICAL PHYSICS

specify circuit with sources



choose set of independent variables




constitutive relations + Kirchhoff's laws



solve for currents and voltages in circuit

example : RCL circuit

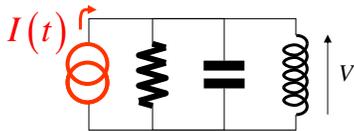

current thru inductance ϕ / L

current thru resistance $\dot{\phi} / R$

current thru capacitance $C\ddot{\phi}$

$\phi(t)$: flux thru inductance
 $\dot{\phi}(t)$: voltage V across inductance

$$C\ddot{\phi} + \frac{\dot{\phi}}{R} + \frac{\phi}{L} = I(t)$$

ETC...

08-l-12a

OUTLINE

1. Review of classical radio-frequency circuits
2. Quantum information processing
3. Quantum-mechanical LC oscillator
4. A non-dissipative, non-linear element: the Josephson junction
5. Energy levels and transitions of the Cooper Pair Box
6. Summary of questions addressed by this course

08-L-5b

THE POWER OF QUANTUM SUPERPOSITION

REGISTER WITH N=10 BITS:

0000000000

0000000001

0000000010

⋮ ⋮ ⋮
⋮ ⋮ ⋮
⋮ ⋮ ⋮

1111111110

1111111111

$2^N = 1024$ POSSIBLE CONFIGURATIONS

classically, can store and work only on
one number between 0 et 1023

“quantally”, can store and work on an
arbitrary superposition of these numbers!

$$|\Psi\rangle = \alpha_0 |0\rangle + \alpha_1 |1\rangle + \alpha_2 |2\rangle + \dots + \alpha_{2^N-1} |2^N - 1\rangle$$

08-L-13a

QUANTUM PARALLELISM

suppose a function $f \quad j \in \{0,1023\} \rightarrow n = f(j) \in \{0,1023\}$

Classically, need 1000×10 -bit registers (10,000 bits) to store information about this function and to work on it.

Quantum-mechanically, a 20-qubit register can suffice!

$$|\Psi\rangle = \frac{1}{2^{N/2}} \sum_{j=0}^{2^N-1} |j\rangle |f(j)\rangle$$

Function encoded in a superposition of states of register

08-I-14


OUTLINE

1. Review of classical radio-frequency circuits
2. Quantum information processing
3. Quantum-mechanical LC oscillator
4. A non-dissipative, non-linear element: the Josephson junction
5. Energy levels and transitions of the Cooper Pair Box
6. Summary of questions addressed by this course

08-I-5c

A CIRCUIT BEHAVING QUANTUM-MECHANICALLY AT THE LEVEL OF CURRENTS AND VOLTAGES ?

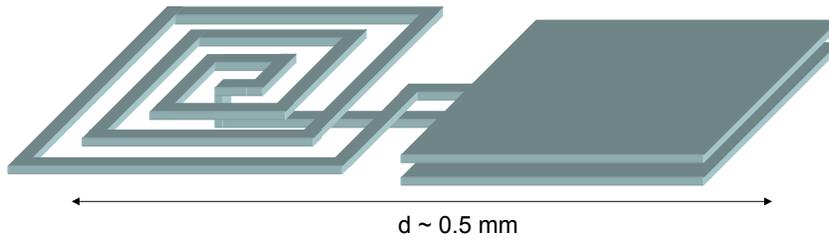SIMPLEST EXAMPLE: SUPERCONDUCTING LC OSCILLATOR CIRCUIT




MICROFABRICATION → $L \sim 3 \text{ nH}$, $C \sim 1 \text{ pF}$, $\omega_r / 2\pi \sim 5 \text{ GHz}$
 $d \ll \lambda$: LUMPED ELEMENT REGIME

SUPERCONDUCTIVITY → ONLY ONE COLLECTIVE VARIABLE
 INCOMPRESSIBLE ELECTRONIC FLUID SLOSHES BETWEEN PLATES.
 NO INTERNAL DEGREES OF FREEDOM.

08-I-15c

DEGREE OF FREEDOM IN ATOM vs CIRCUIT: SEMI-CLASSICAL DESCRIPTION

Rydberg atom

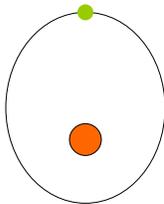

Superconducting LC oscillator




08-I-16


DEGREE OF FREEDOM IN ATOM vs CIRCUIT

semiclassical picture

Rydberg atom

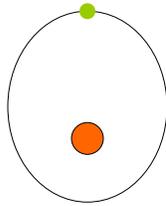

Superconducting LC oscillator

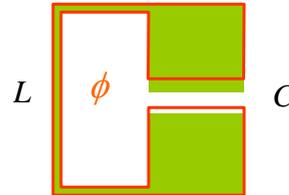



2 possible correspondences:

charge dynamics	{	velocity of electron →	current through inductor
		force on electron →	voltage across capacitor
field dynamics	{	velocity of electron →	voltage across capacitor
		force on electron →	current through inductor



08-I-16b



FLUX AND CHARGE IN LC OSCILLATOR

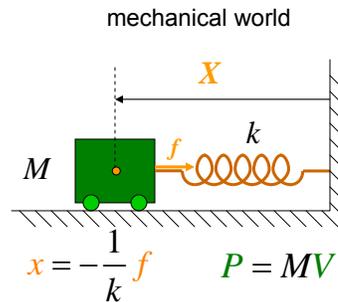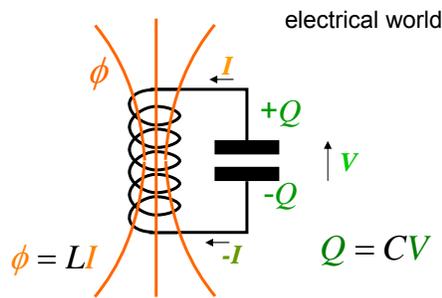



{	position variable:	ϕ	↔	x	$x = X - X_0$
	momentum variable:	Q	↔	P	
{	generalized force on mass:	I	↔	f	↑ equilibrium position of spring
	generalized velocity:	V	↔	V	
{	generalized mass:	C	↔	M	
	generalized spring constant:	$1/L$	↔	k	

08-I-17a

HAMILTONIAN FORMALISM

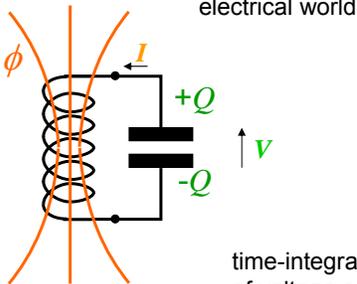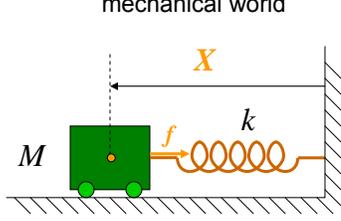electrical world	mechanical world
	
<p>time-integral of voltage on inductor = flux in inductor</p> <p>charge on capacitor</p>	<p>elongation of spring</p> <p>momentum of mass</p>
$H(\phi, Q) = \frac{Q^2}{2C} + \frac{\phi^2}{2L}$ <p style="text-align: center;">conjugate variables</p>	$H(x, P) = \frac{P^2}{2M} + \frac{kx^2}{2}$ <p style="text-align: center;">conjugate variables</p>
08-I-18	

HAMILTON'S EQUATION OF MOTION

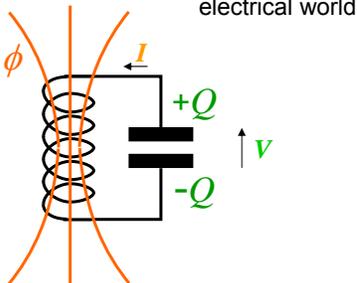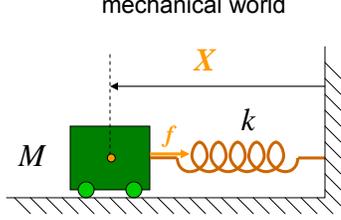electrical world	mechanical world
	
$\left. \begin{aligned} \dot{\phi} &= \frac{\partial H}{\partial Q} = \frac{Q}{C} \\ \dot{Q} &= -\frac{\partial H}{\partial \phi} = -\frac{\phi}{L} \end{aligned} \right\} \Rightarrow \omega_r = \sqrt{\frac{1}{LC}}$	$\left. \begin{aligned} \dot{x} &= \frac{\partial H}{\partial P} = \frac{P}{M} \\ \dot{P} &= -\frac{\partial H}{\partial x} = -kx \end{aligned} \right\} \Rightarrow \omega_r = \sqrt{\frac{k}{M}}$
08-I-19	

FROM CLASSICAL TO QUANTUM PHYSICS: CORRESPONDENCE PRINCIPLE

$$X \text{ and } P \text{ are conjugate variables } \begin{cases} X \rightarrow \hat{X} & \text{position operator} \\ P \rightarrow \hat{P} & \text{momentum operator} \end{cases}$$


$$H(X, P) \rightarrow \hat{H}(\hat{X}, \hat{P}) \quad \text{hamiltonian operator}$$

$$\frac{\partial A \partial B}{\partial X \partial P} - \frac{\partial A \partial B}{\partial P \partial X} = \{A, B\}_{PB} \rightarrow [\hat{A}, \hat{B}] / i\hbar \quad \text{commutator}$$

$$\begin{array}{c} \uparrow \\ \text{Poisson bracket} \end{array} \rightarrow \{X, P\}_{PB} = 1 \rightarrow [\hat{X}, \hat{P}] = i\hbar \quad \begin{array}{l} \text{position and} \\ \text{momentum} \\ \text{operators do} \\ \text{not commute} \end{array}$$

08-I-20

FLUX AND CHARGE DO NOT COMMUTE

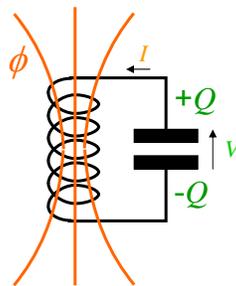

$$[\hat{\phi}, \hat{Q}] = i\hbar$$



This fundamental result arises from the correspondence principle applied to the LC oscillator

Not every pairs of variables can satisfy such commutation relation. As *A.J. Leggett* once remarked in a seminar presenting his seminal work on macroscopic quantum mechanics: " We cannot quantize the equations of the stock market!"

We can also obtain this result from quantum field theory through the commutation relations of the electric and magnetic field. See third lecture in this course.

08-I-21

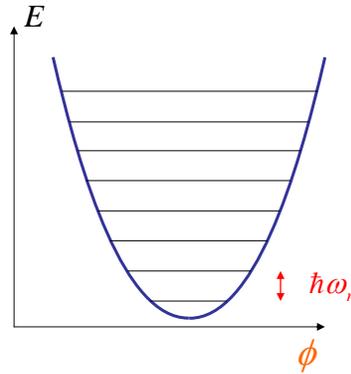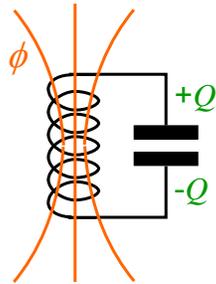LC CIRCUIT AS QUANTUM HARMONIC OSCILLATOR



$$\hat{H} = \hbar\omega_r \left(\hat{a}^\dagger \hat{a} + \frac{1}{2} \right)$$

$$\hat{a} = \frac{\hat{\phi}}{\phi_r} + i \frac{\hat{Q}}{Q_r}; \quad \hat{a}^\dagger = \frac{\hat{\phi}}{\phi_r} - i \frac{\hat{Q}}{Q_r}$$



$$\phi_r = \sqrt{2\hbar\omega_r L}$$

$$Q_r = \sqrt{2\hbar\omega_r C}$$

← annihilation and creation operators

08-L-22

THERMAL EXCITATION OF LC CIRCUIT

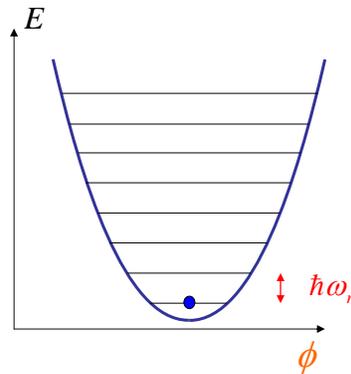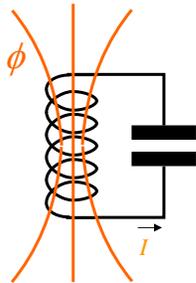


Can place the circuit
in its ground state


$$5 \text{ GHz} \rightarrow \hbar\omega_r \gg k_B T \leftarrow 10 \text{ mK}$$

08-L-22a

WAVEFUNCTIONS OF LC CIRCUIT

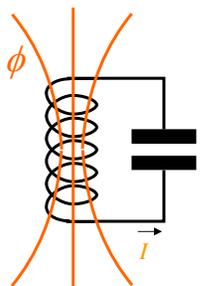


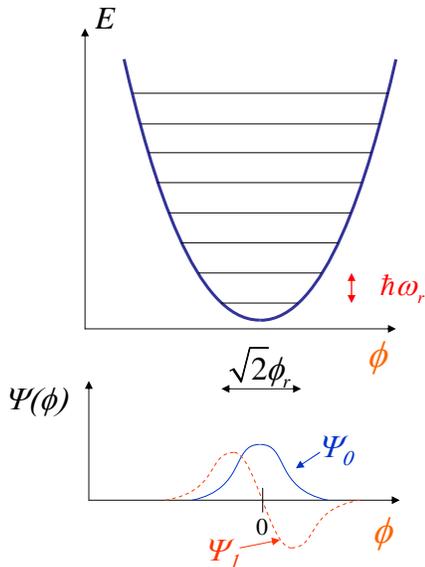In every energy eigenstate,
(photon state)
current flows in opposite
directions simultaneously!




08-1-23

EFFECT OF DAMPING

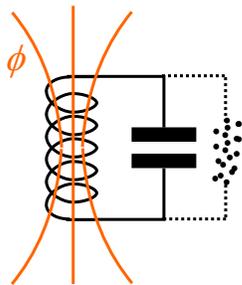

important:
negligible dissipation

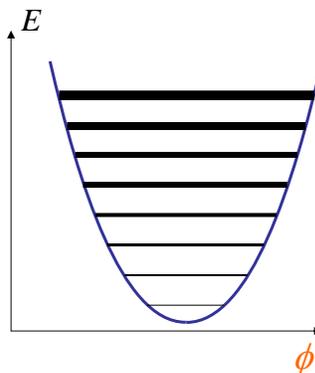

dissipation broadens energy levels


$$E_n = \hbar\omega_r \left[n \left(1 + \frac{i}{2Q} \right) + \frac{1}{2} \right]$$

$$Q = RC\omega_r$$

see
why
later

08-1-24

ALL TRANSITIONS ARE DEGENERATE

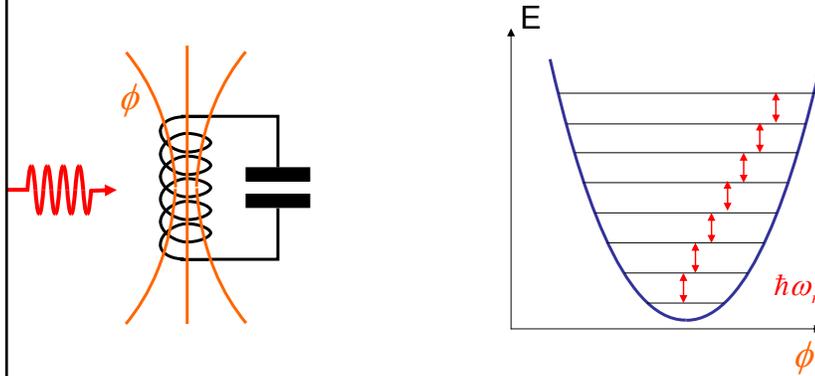


CANNOT STEER THE SYSTEM TO AN ARBITRARY STATE
IF PERFECTLY LINEAR

08-1-25

NEED NON-LINEARITY TO FULLY REVEAL QUANTUM MECHANICS

Potential energy

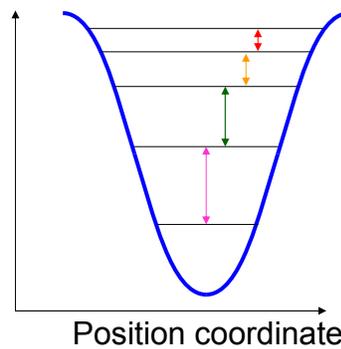



08-1-26

OUTLINE

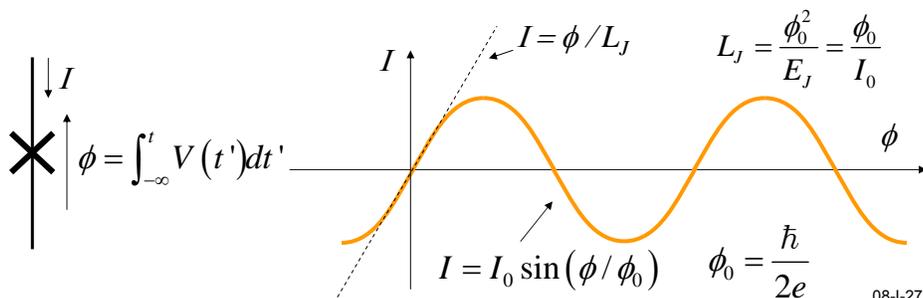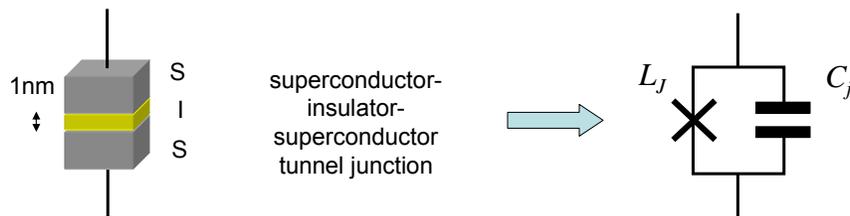1. Review of classical radio-frequency circuits
2. Quantum information processing
3. Quantum-mechanical LC oscillator
4. A non-dissipative, non-linear element: the Josephson junction
5. Energy levels of the Cooper Pair Box
6. Summary of questions addressed by this course


08-I-5d

JOSEPHSON JUNCTION PROVIDES A NON-LINEAR INDUCTOR



08-I-27b

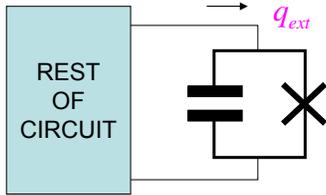COUPLING PARAMETERS OF THE JOSEPHSON JUNCTION "ATOM"



THE hamiltonian: (we mean it!)
$$\hat{H}_j = \frac{1}{2C_j} \left(\hat{Q} - q_{ext} \right)^2 - E_J \cos \frac{2e\hat{\phi}}{\hbar}$$

Comparable with lowest order model for hydrogen atom \rightarrow

$$\hat{H} = \frac{1}{2m_e} \left(\hat{p} - \frac{eA}{\hbar} \right)^2 - \frac{e^2}{4\pi\epsilon_0} \frac{1}{\hat{r}}$$

TWO ENERGY SCALES

Two dimensionless variables:

$$\hat{\phi} = \frac{2e\hat{\phi}}{\hbar} \quad \hat{N} = \frac{\hat{Q}}{2e} \quad \Rightarrow \quad [\hat{\phi}, \hat{N}] = i$$

Hamiltonian becomes :

$$\hat{H}_j = 8E_C \frac{(\hat{N} - N_{ext})^2}{2} - E_J \cos \hat{\phi}$$

Coulomb charging energy for 1e

$$E_C = \frac{e^2}{2C_j}$$

reduced offset charge

$$N_{ext} = \frac{q_{ext}}{2e}$$

Josephson energy

$$E_J = \frac{1}{8} \mathcal{N} \mathcal{T} \Delta$$

barrier transp^{cy} \leftarrow gap
 \uparrow
 # cond^{ion} channels
 valid for opaque barrier

HARMONIC APPROXIMATION

$$\widehat{H}_j = 8E_C \frac{(\widehat{N} - N_{ext})^2}{2} - E_J \cos \widehat{\phi}$$




$$\widehat{H}_{j,h} = 8E_C \frac{(\widehat{N} - N_{ext})^2}{2} + E_J \frac{\widehat{\phi}^2}{2}$$

Josephson plasma frequency $\omega_p = \frac{\sqrt{8E_C E_J}}{\hbar}$

Spectrum independent of DC value of N_{ext}

08-I-30

credit I. Siddiqi and F. Pierre

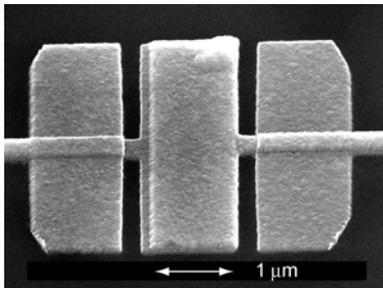


$$E_J \sim 50\text{K}$$

$$\omega_p \sim 30\text{-}40\text{GHz}$$

$$E_J \sim 0.5\text{K}$$

TUNNEL JUNCTIONS IN REAL LIFE

credit L. Frunzio and D. Schuster

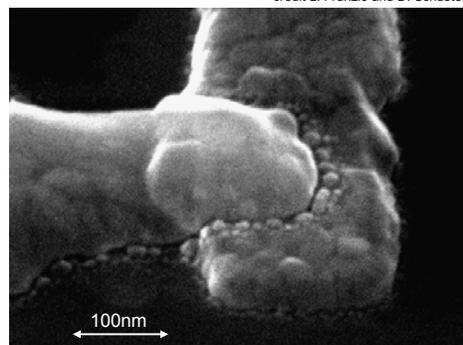


08-I-31



OUTLINE

1. Review of classical radio-frequency circuits
2. Quantum information processing
3. Quantum-mechanical LC oscillator
4. A non-dissipative, non-linear element: the Josephson junction
5. Energy levels and transitions of the Cooper Pair Box
6. Summary of questions addressed by this course

08-I-5e


EFFECTIVE POTENTIAL OF 3 BIAS SCHEMES

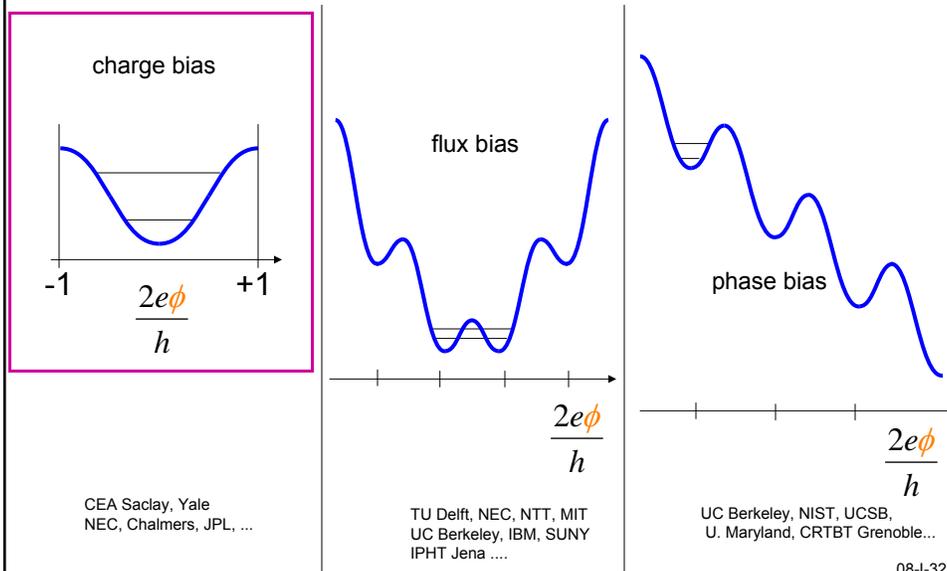

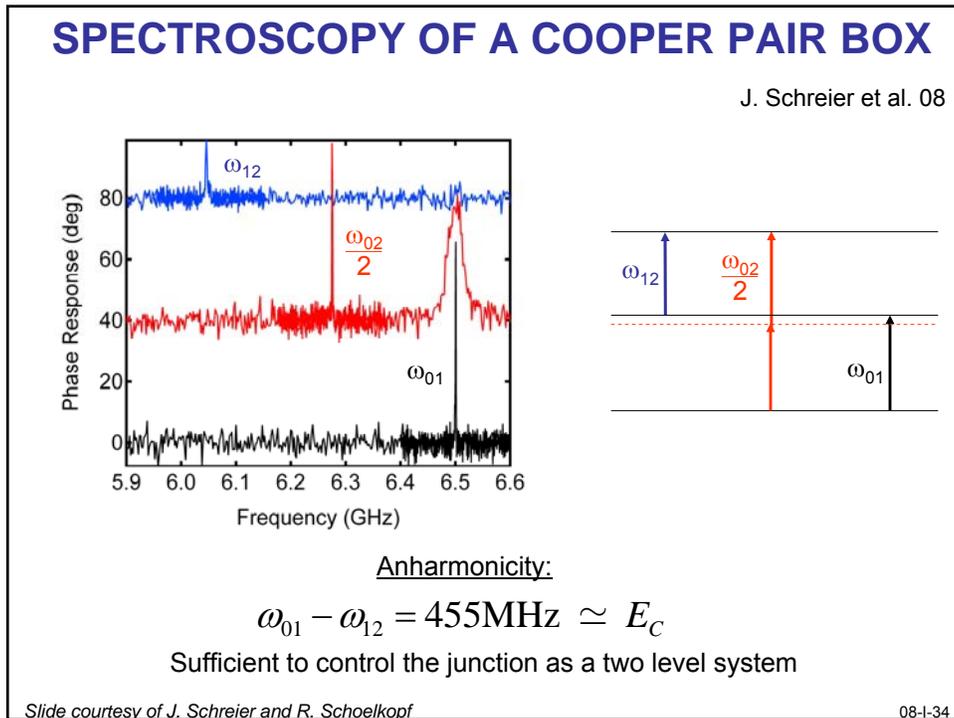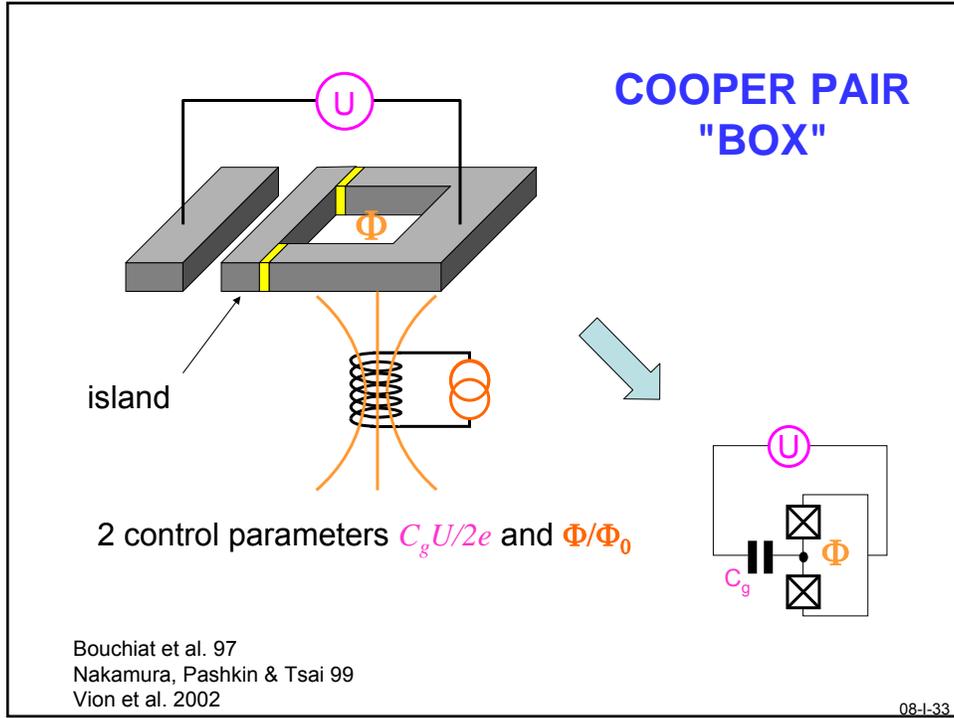

ANHARMONICITY vs CHARGE SENSITIVITY

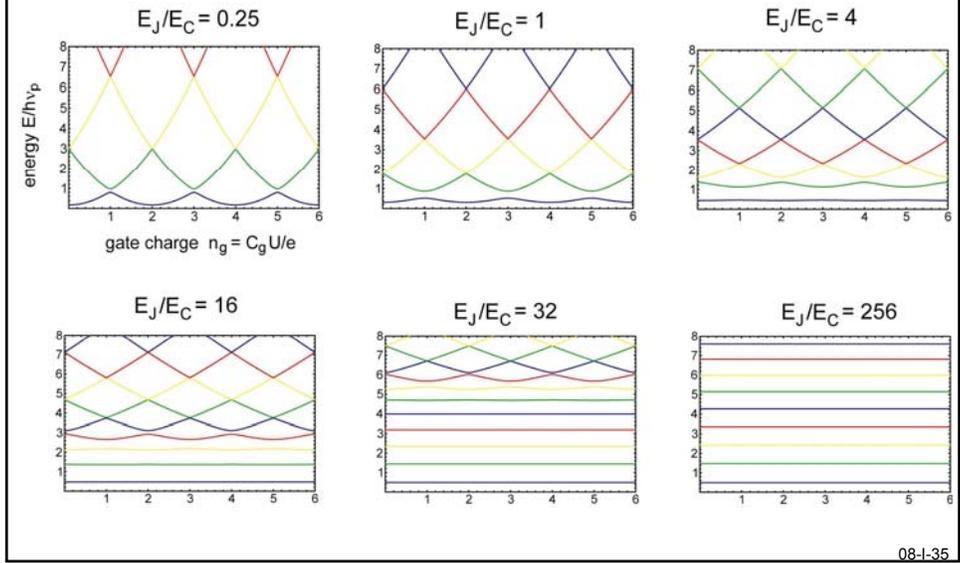Cooper pair box soluble in terms of Mathieu functions (A. Cottet, PhD thesis, Orsay, 2002)



ANHARMONICITY vs CHARGE SENSITIVITY IN THE LIMIT $E_C/E_J \ll 1$


anharmonicity:
$$\frac{\omega_{12} - \omega_{01}}{(\omega_{12} + \omega_{01})/2} \rightarrow \sqrt{\frac{E_C}{8E_J}}$$

peak-to-peak charge modulation amplitude of level m:

$$\epsilon_m \rightarrow (-1)^m E_C \frac{2^{4m+5}}{m!} \sqrt{\frac{2}{\pi}} \left(\frac{E_J}{2E_C}\right)^{\frac{m}{2} + \frac{3}{4}} e^{-\sqrt{8E_J/E_C}}$$

J. Koch et al. 07

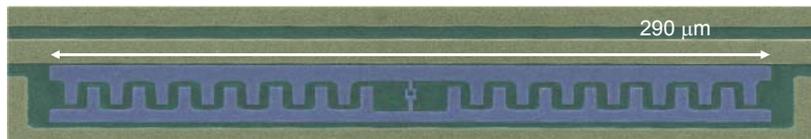TRANSMON: SHUNT JUNCTION WITH CAPACITANCE



Courtesy of J. Schreier and R. Schoelkopf

08-I-36


OUTLINE

1. Review of classical radio-frequency circuits
2. Quantum information processing
3. Quantum-mechanical LC oscillator
4. A non-dissipative, non-linear element: the Josephson junction
5. Energy levels and transitions of the Cooper Pair Box
6. Summary of questions addressed by this course

08-I-5f

**CAN WE BUILD ALL THE QUANTUM INFORMATION
PROCESSING PRIMITIVES OUT OF SIMPLE CIRCUITS
AND CONNECT THESE CIRCUITS TO PERFORM ANY
DESIRED FUNCTION?**

08-I-37

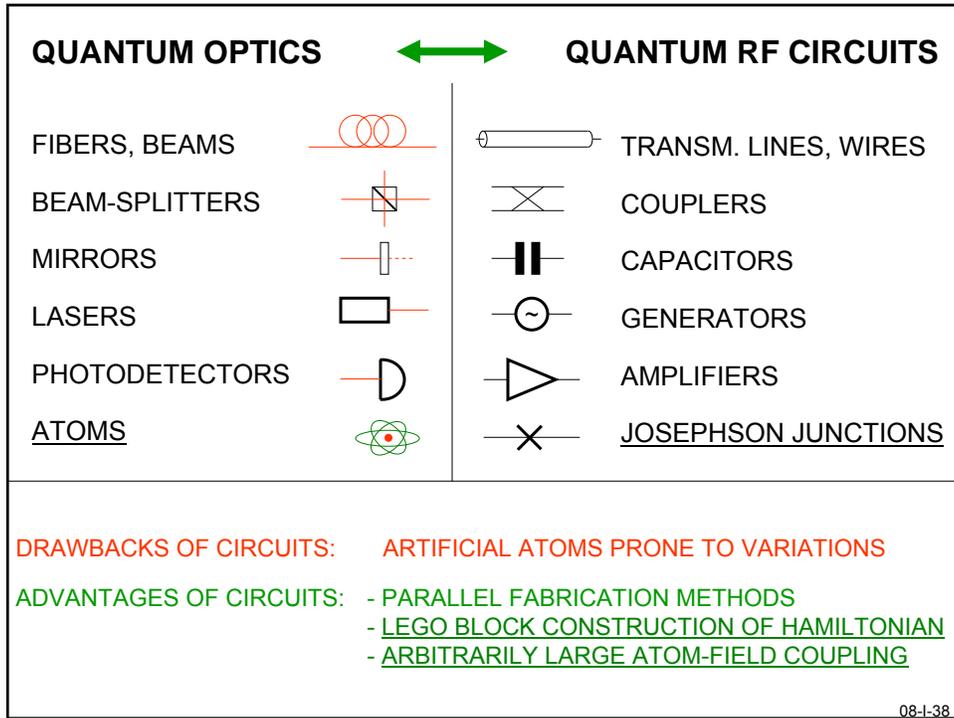

**HOW DO WE TRANSLATE FROM THE LANGUAGE
 OF ELECTRICAL SIGNALS COUPLED
 IN A NON-LINEAR CIRCUIT
 INTO THE LANGUAGE OF
 PHOTONS INTERACTING WITH ATOMS
 (EMISSION, ABSORPTION, SCATTERING, DETECTION)?**

**HOW DO WE DO TREAT QUANTUM-MECHANICALLY
 A DISSIPATIVE, NON-LINEAR, OUT-OF-EQUILIBRIUM
 ENGINEERED SYSTEM?**

08-I-39

SELECTED BIBLIOGRAPHY

Books

- Braginsky, V. B., and F. Y. Khalili, "Quantum Measurements" (Cambridge University Press, Cambridge, 1992)
- Cohen-Tannoudji, C., Dupont-Roc, J. and Grynberg, G., "Atom-Photon Interactions" (Wiley, New York, 1992)
- Haroche, S. and Raimond, J-M., "Exploring the Quantum" (Oxford University Press, 2006)
- Mallat, S. M., "A Wavelet Tour of Signal Processing" (Academic Press, San Diego, 1999)
- Nielsen, M. and Chuang, I., "Quantum Information and Quantum Computation" (Cambridge, 2001)
- Pozar, D. M., "Microwave Engineering" (Wiley, Hoboken, 2005)
- Tinkham, M., "Introduction to Superconductivity" (2nd edition, Dover, New York, 2004)

Review articles

- Courty J. and Reynaud S., Phys. Rev. A **46**, 2766-2777 (1992)
- Devoret M. H. in "Quantum Fluctuations", S. Reynaud, E. Giacobino, J. Zinn-Justin, Eds. (Elsevier, Amsterdam, 1997) p. 351-385
- Makhlin Y., Schön G., and Shnirman A., Nature (London) **398**, 305 (1999).
- Devoret M. H., Wallraff A., and Martinis J. M., e-print cond-mat/0411174
- Blais A., Gambetta J., Wallraff A., Schuster D. I., Girvin S., Devoret M.H., Schoelkopf R.J. Phys. Rev. (2007) A **75**, 032329

Articles

- Koch J, et al. Phys. Rev. A **76**, 042319 (2007)
- Schreier J., et al, .arXiv:0712.3581, J. A. Schreier, et al., Phys. Rev. B **77**, 180502(R) (2008)
- Houck A. A., et al. arXiv:0803.4490, A. A. Houck, et al., Phys. Rev. Lett. **101**, 080502 (2008)

08-140

END OF LECTURE